

CS1101: Lecture 23

The Digital Logic Level: Gates

Dr. Barry O'Sullivan
b.osullivan@cs.ucc.ie



Course Homepage
<http://www.cs.ucc.ie/~osullb/cs1101>

- A Six-Level Computer
- Gates
- Transistors
- Gates from Transistors
- The Three Simple Gates
- From Three to Five Simple Gates
- Building Computers
- **Reading:** Tanenbaum, Chapter 3, Section 1

Department of Computer Science, University College Cork

Department of Computer Science, University College Cork

1

CS1101: Systems Organisation

The Digital Logic Level

A Six-Level Computer

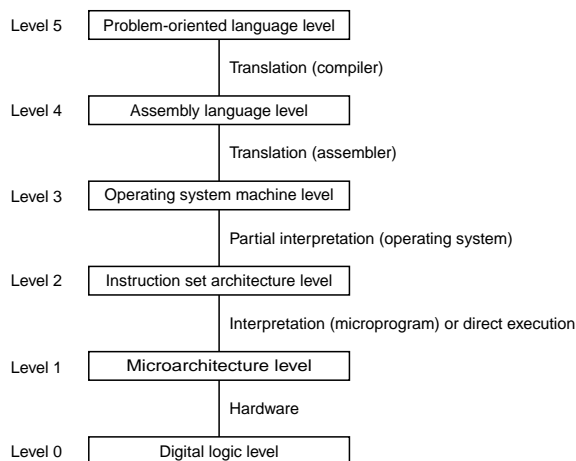


Figure 1-2. A six-level computer.

CS1101: Systems Organisation

The Digital Logic Level

Introduction

- The Digital Logic Level is at the bottom of our hierarchical model.
- Digital circuits are constructed from a small set of primitive elements
- A special two-valued algebra is used to analyse these circuits
- Boolean Algebra
- So how does it all work?

- A digital circuit is one in which only two logical values are present – 0 and 1;
- Typically, a signal between 0-1 volts represents a binary 0, a signal between 2-5 volts represents a binary 1,
- Tiny electronic devices, called **gates**, can compute various functions over these two-valued signals;
- These gates form the hardware basis on which all digital computers are built.
- How is a gate implemented?

- All modern digital logic rests on the fact that a transistor can be made to operate as a very fast binary switch;
- The transistor has 3 connections to the outside world: the **collector**, the **base** and the **emitter**;
- The input voltage is applied to the base
- When the input voltage is **low**, the transistor voltage is **high**
- When the input voltage is **high**, the transistor voltage is **low**
- Thus, this circuit is an **inverter**
- We can build all logic gates with this!!!

Gates from Transistors

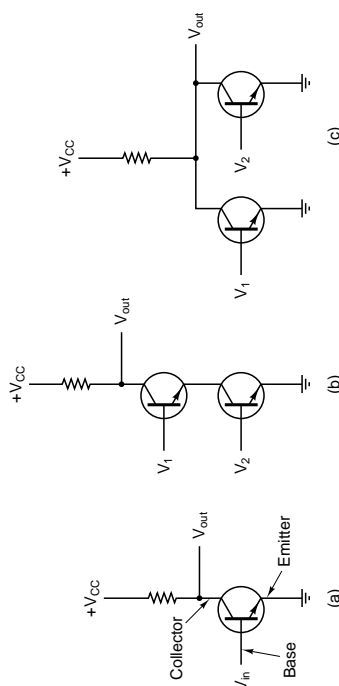


Figure 3-1: (a) A transistor inverter, (b) A NAND gate (c) A NOR gate

The Three Simple Gates

- The circuits given previously form the three simplest gates: NOT, NAND and NOR;
- NOT gates are often called **inverters**
- If we adopt the convention that “high” means logical 1 and “low” means logical 0, we can express the output value as a function of the input values
- Icons for the simplest functions will be presented next.

From Three to Five Simple Gates

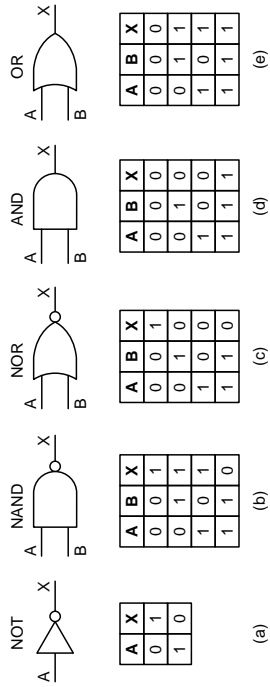


Figure 3-2: The symbols and functional behaviour for the five basic gates

Department of Computer Science, University College Cork

Building Computers

- It should be clear that NAND and NOR gates can be built with two transistors, whereas AND and OR gates require three each.
- Thus, many computers are built from NAND and NOR gates rather than the familiar AND and OR gates;
- These gates can have more than two inputs, but seldom have more than 8.